


INDUCTANCE


The magnetic flux through a coil  is proportional to the current I traveling through the coil. We define self-inductance with that in mind,

$$\Phi_B = L I$$

↑ flux in coil ↑ proportionality constant ← current

L is called the inductance, its units are **H** for Henry

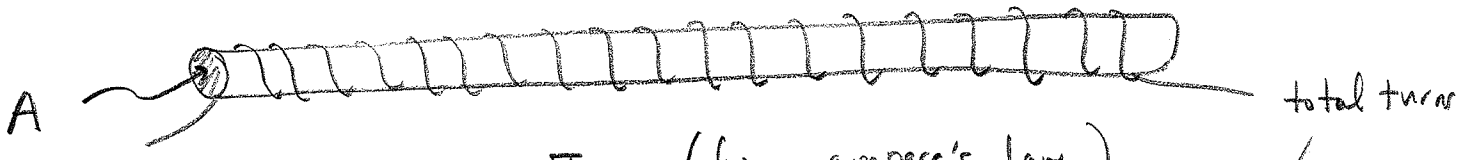E79 For a solenoid (long) with area A and $n = \frac{\text{turns}}{\text{length}}$



$$B = \mu_0 n I \quad (\text{from ampere's Law})$$

$$\Phi_B = N B A = N (\mu_0 n I) A \quad \text{where } n = \frac{N}{l}$$

↑ length

$$L = \frac{\Phi_B}{I} = \frac{\mu_0 n N I A}{I}$$

$$\Rightarrow L = \mu_0 n N A \quad (\text{note } N = n l)$$

$$\Rightarrow \boxed{L = \mu_0 n^2 A l}$$

The reason for the " N " in Φ_B is that the flux goes through each and every one of the N -loops which make up the solenoid.

Remark: $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

Inductors and Circuits

$$\Phi_B = L I$$


$$\frac{d\Phi_B}{dt} = \frac{d}{dt}(L I) = L \frac{dI}{dt}$$

for most inductors, the geometry is fixed
so L doesn't change with time.

But, $\frac{d\Phi_B}{dt} = -\mathcal{E} \quad \therefore \quad \underline{\mathcal{E} = -L \frac{dI}{dt}}$ } resists
instant.
change
in
current

If the inductor has resistance r then
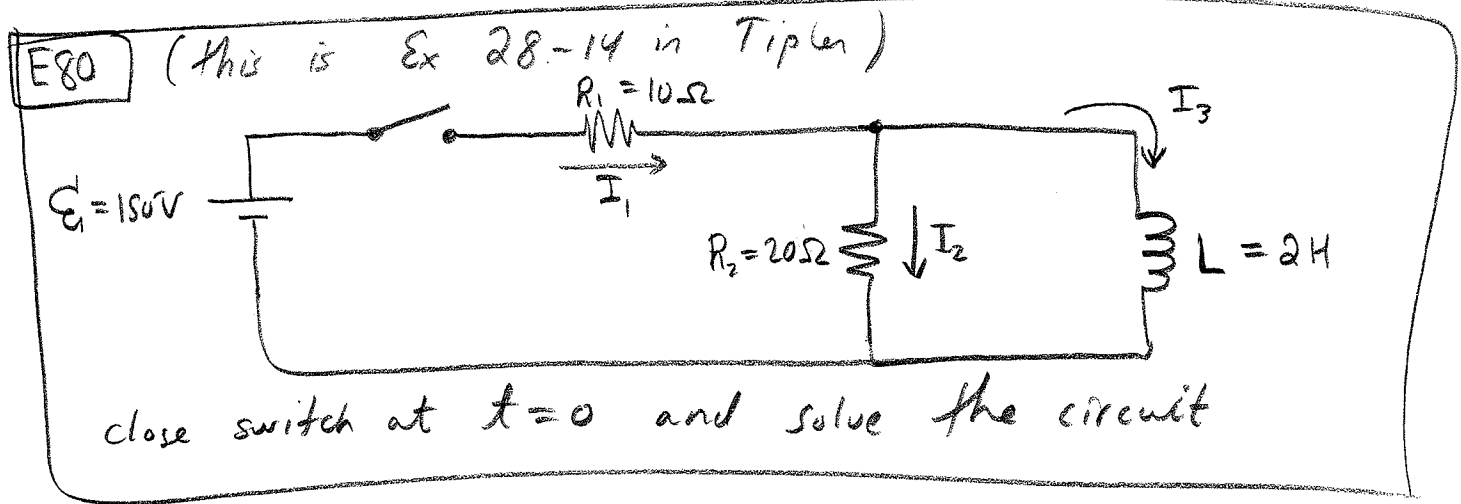
$$\underline{\Delta V = \mathcal{E} - I r = -L \frac{dI}{dt} - I r}$$



$$\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$


$$I_2 R_2 = -L \frac{dI_3}{dt}$$

$$I_1 = I_2 + I_3$$

challenge, solve.

(we'll analyze $t=0$ and $t \rightarrow \infty$ in lecture)

E81

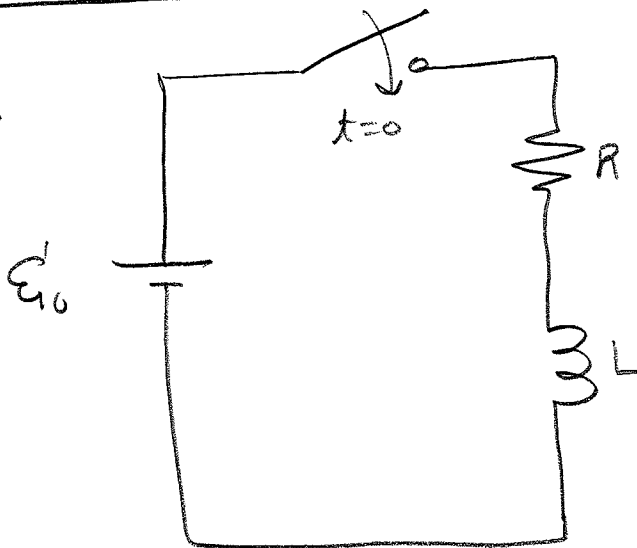

close switch then
find $I(t)$ (CHAD)

$$E_0 - IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} + \frac{R}{L} I = \frac{E_0}{L}$$

$$\Rightarrow I(t) = C_1 e^{-\frac{Rt}{L}} + \frac{E_0}{R}$$

$$I(0) = C_1 + \frac{E_0}{R} = 0$$

initial current zero.

$$\therefore C_1 = -E_0/R$$

$$\Rightarrow I(t) = \frac{E_0}{R} (1 - e^{-t/\tau})$$

where $\tau = \frac{L}{R}$

time constant
for RL circuit.

The eqⁿ above is for $t \geq 0$
naturally $I(t) = 0$ for $t < 0$.

Remark: Mutual Inductance is defined for some pair of circuits. It describes how the current in circuit 1 creates a magnetic flux in circuit 2. Generically,

$$\Phi_B \text{ in circuit \#2 due to } I_1 = M_{12} I_1$$

↑
mutual inductance

Likewise, one could define


$$\Phi_B \text{ in circuit \#1 due to } I_2 = M_{21} I_2$$

It turns out that $M_{12} = M_{21}$ in general.
(I didn't assign any work on this)



Magnetic Energy
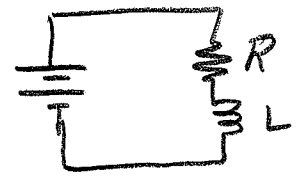
$$\mathcal{E}_0 - IR - L \frac{dI}{dt} = 0 \quad \text{for}$$



$$\Rightarrow \underbrace{\mathcal{E}_0 I}_{\text{rate energy supplied to circuit}} = \underbrace{I^2 R}_{\text{energy lost in R per time}} + \underbrace{LI \frac{dI}{dt}}_{\text{energy per time stored in L}}$$

$$\frac{dU}{dt} = LI \frac{dI}{dt} \Rightarrow dU = LI dI$$
$$\Rightarrow \boxed{U = \frac{1}{2} LI^2}$$

energy stored in inductor proportional to square of I flowing through I.


Energy Density in Magnetic Field

(110)

As I flows through mm it sets-up a magnetic field with energy $U = \frac{1}{2} L I^2$.

For a solenoid we can calculate more;

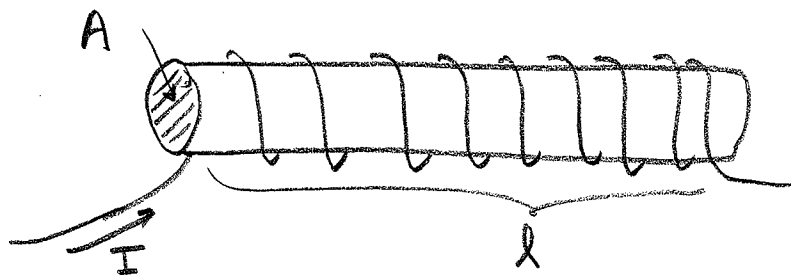E82 deriving energy density from Solenoid Example,



we derived this previous lecture.

$$B = \mu_0 n I \quad \text{and} \quad L = \mu_0 n^2 A l$$

$$\text{Volume} = A l$$

$$\frac{U}{\text{Vol.}} = \frac{\frac{1}{2} L I^2}{A l} = \frac{\frac{1}{2} \mu_0 n^2 A l I^2}{A l} = \frac{1}{2} \mu_0 n^2 \left(\frac{B}{\mu_0 n} \right)^2$$

(Note: An arrow labeled "solving for B" points from the fraction $\frac{B}{\mu_0 n}$ in the final term back to the B in the equation above.)

$$\therefore \frac{\text{Energy in B-field}}{\text{Volume}} = \frac{1}{2 \mu_0} B^2$$

E83 In retrospect, a capacitor has

$$\frac{\text{Energy in E-field}}{\text{Volume}} = \frac{1}{2} \epsilon_0 E^2$$

To see this recall $U = \frac{1}{2} C V^2$ and $V = E d$
and $C = \frac{A \epsilon_0}{d}$ and $\text{Vol} = A d$ so

$$\frac{U}{\text{Vol}} = \frac{\frac{1}{2} C V^2}{A d} = \frac{\frac{1}{2} A \epsilon_0 (E d)^2}{A d^2} = \frac{1}{2} \epsilon_0 E^2$$

E82 & E83 actually reveal general formulas for energy density due to the Electric & Magnetic Fields.

(111)

You can derive the same $\frac{1}{2\mu_0} B^2$ or $\frac{\epsilon_0}{2} E^2$ energy dependence for constant B or E fields filling other geometries. Generally you have $\frac{dU}{dV} = \frac{1}{2\mu_0} B^2$ or $\frac{dU}{dV} = \frac{\epsilon_0}{2} E^2$

So to find total energy if B or E varies you do some volume integral


$$U_{\text{TOTAL IN } V} = \iiint_V \left(\frac{1}{2\mu_0} B^2 + \frac{\epsilon_0}{2} E^2 \right) dV$$

(however since calculus III is not prereq. we'll abstain from explicit computation of such integrals, fascinating as they may be...)

LC CIRCUIT

112

E84

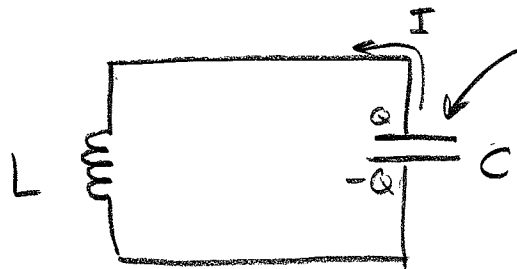

initially charged to V_0
find $I(t)$ for $t > 0$.
(assume $I(0) = 0$.)

$$I = -\frac{dQ}{dt}$$

$$-L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$\Rightarrow -L \frac{d}{dt} \left(-\frac{dQ}{dt} \right) + \frac{Q}{C} = 0$$

$$\frac{d^2 Q}{dt^2} + \frac{Q}{LC} = 0$$

well-known
DE₂!

$$\rightarrow Q(t) = Q_0 \cos(\omega t + \phi_0), \quad \omega = \sqrt{\frac{1}{LC}}$$

$$I(t) = -\frac{dQ}{dt} = \omega Q_0 \sin(\omega t + \phi_0)$$

Note, $V_0 = \frac{Q_0}{C} \Rightarrow \underline{Q_0 = V_0 C}$

Also $I(0) = 0 = \omega Q_0 \sin(\phi_0) \Rightarrow \underline{\text{choose } \phi_0 = 0}$.


Hence $I(t) = \frac{V_0 C}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right)$

$$I(t) = \omega V_0 C \sin(\omega t), \quad \omega = \frac{1}{\sqrt{LC}}$$

Also, for E85 note $Q(t) = C V_0 \cos(\omega t)$

E85

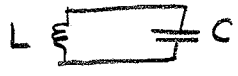Find energy in L or C at time t for E84 circuit



$$U_C = \frac{1}{2C} Q^2 = \frac{1}{2C} (C V_0 \cos(\omega t))^2$$

$$\Rightarrow U_C(t) = \frac{1}{2} C V_0^2 \cos^2(\omega t), \quad \omega = \frac{1}{\sqrt{LC}}$$

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L (\omega V_0 C \sin(\omega t))^2$$


$$= \frac{1}{2} L C^2 \omega^2 V_0^2 \sin^2(\omega t)$$

$$= \frac{1}{2} \frac{LC^2}{LC} V_0^2 \sin^2(\omega t)$$

$$\Rightarrow U_L(t) = \frac{1}{2} C V_0^2 \sin^2(\omega t)$$

Note $U_C + U_L = \frac{1}{2} C V_0^2$ which is precisely the initial energy stored in C. As time goes on the L & C simply pass the energy back and forth w/o end.

E86

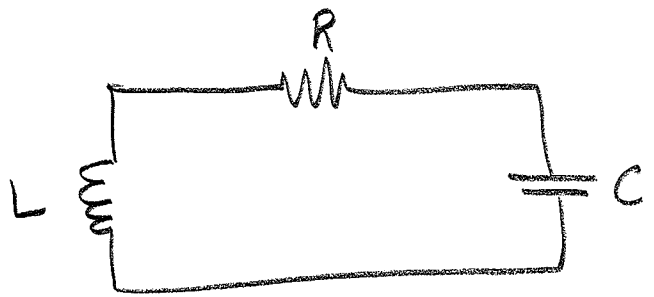

(like spring with friction, same math.)

R=0, SHO.

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = 0$$

$$\Rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

critical damped
under damped